

University of Ottawa

Master of Engineering
Electrical and Computer Engineering

Assignment 1 ELG7132D

Topics in Electronics I: Simulation of Radio Frequency Circuits

Submitted by

Karthik M Prakash
University ID: 300037618

| Contents | Pg.no |
|----------------------------------|--------------|
| 1. Introduction | 3 |
| 2. Circuit Diagram..... | 4 |
| 3. Equivalent Circuit Model..... | 5 |
| 4. G Matrix..... | 6 |
| 5. C Matrix..... | 7 |
| 6. Source Vector..... | 8 |
| 7. Function Vector..... | 9 |
| 8. Nodes and their Indices..... | 10 |

Introduction

The objective is to get familiarized with the HiSPICE- Matlab interface as a tool to used extract the circuit mathematical structures which is done through executing simple commands to access the mathematical constructs describing the circuit.

Circuit Diagram

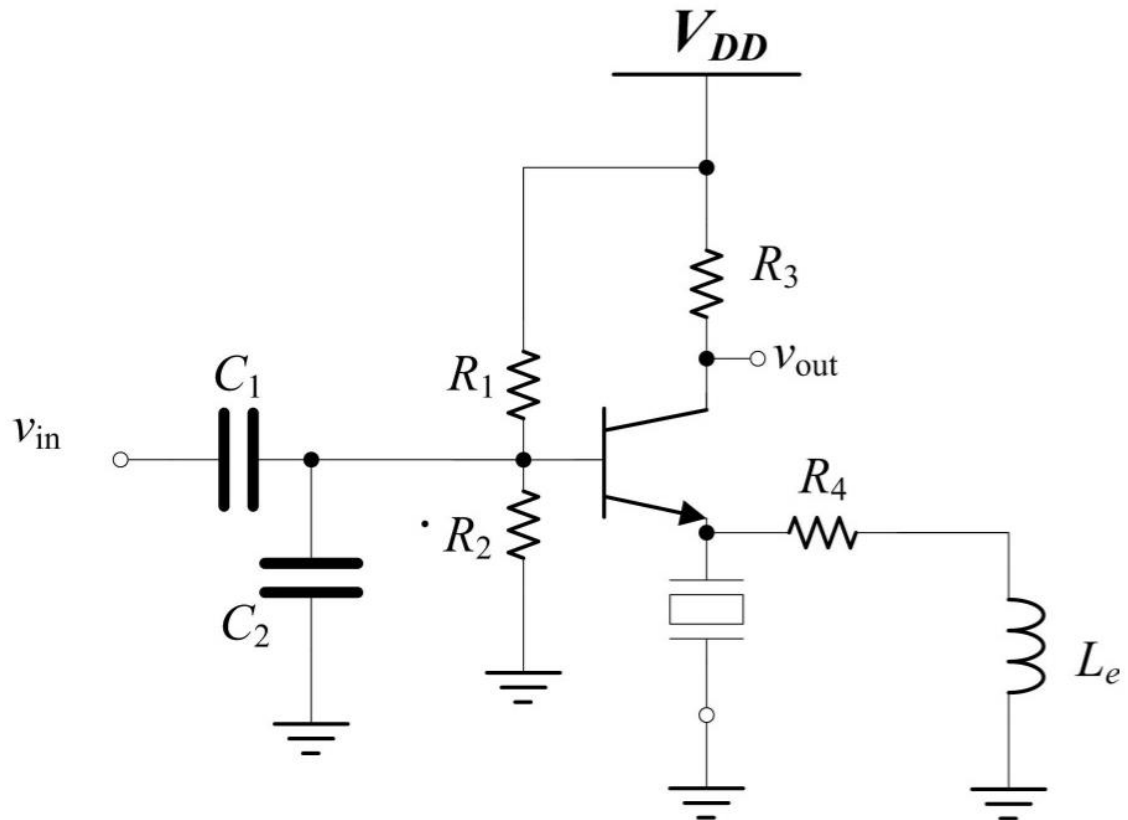


Fig.1 Tuned Amplifier Circuit

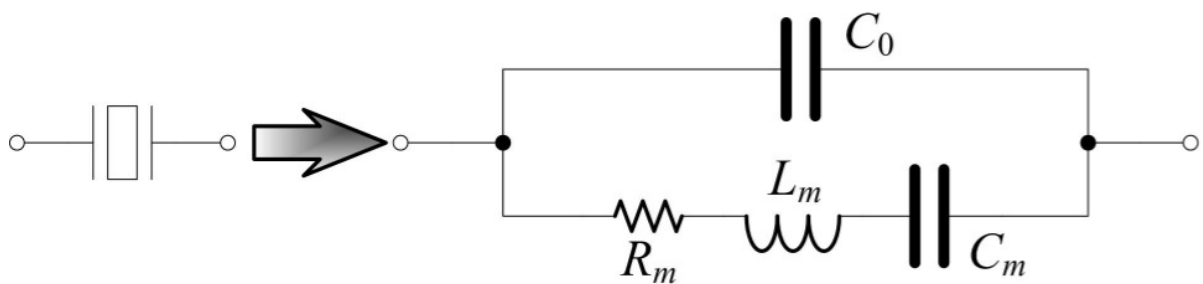


Fig.1.1 Crystal Equivalent model

Equivalent Circuit Model

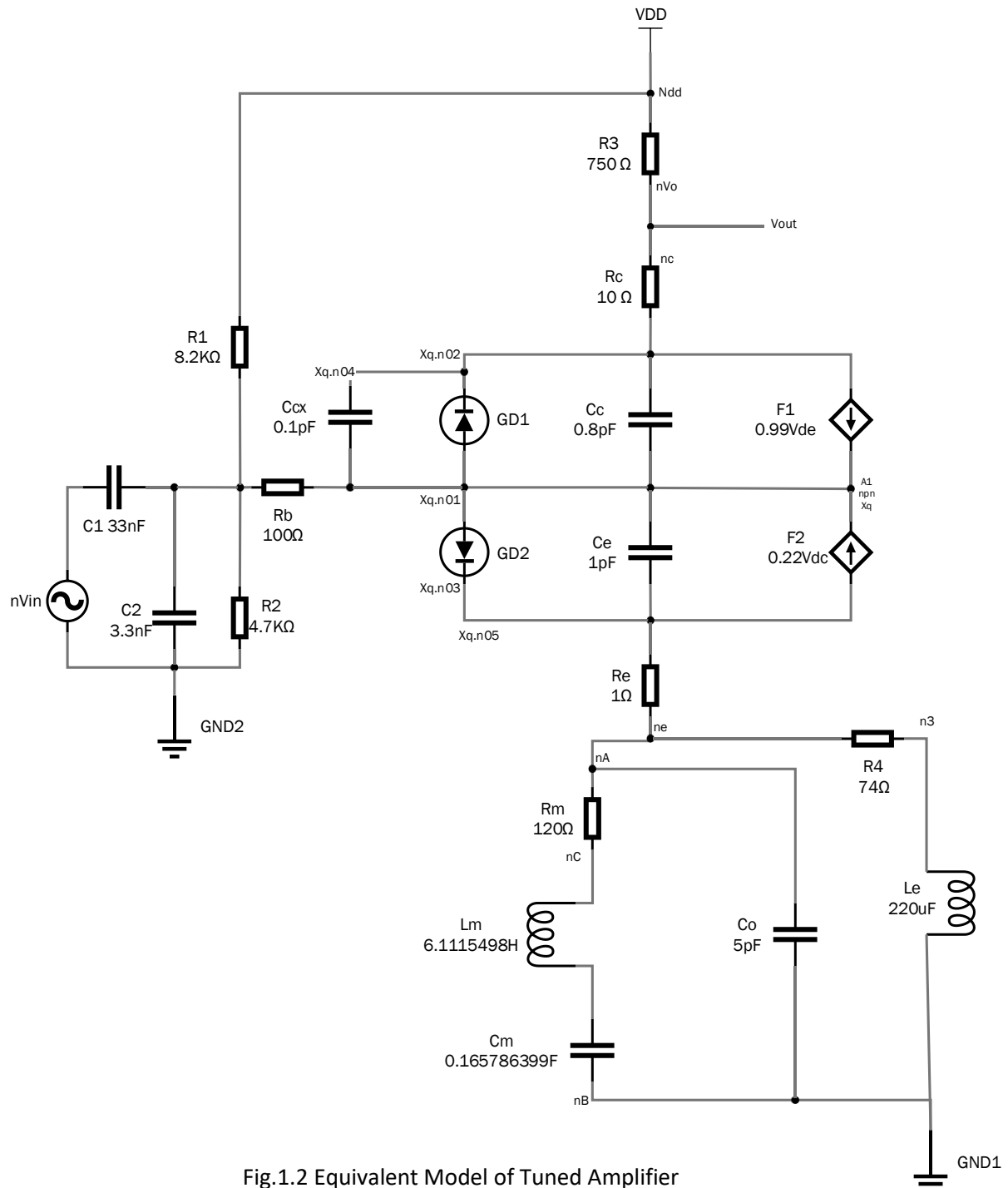


Fig.1.2 Equivalent Model of Tuned Amplifier

G – Matrix

| | | | | | | | | | | | | | | | | | | |
|---------------|---|-----------------------|---------------|----------------------|---------|--------|---------|---|---|---------|---------|--------|---|---|---|-------|-------|----|
| | 0 | $-1/R1$ | $-1/R3$ | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| $1/R1 + 1/R3$ | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| $-1/R1$ | 0 | $-1/R1 + 1/R2 + 1/Rb$ | 0 | 0 | 0 | 0 | $-1/Rb$ | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| $-1/R3$ | 0 | 0 | $1/R3 + 1/Rc$ | 0 | 0 | 0 | 0 | 0 | 0 | $-1/Rc$ | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | $1/Rc + 1/Rm + 1/R4$ | $-1/R4$ | 0 | 0 | 0 | 0 | 0 | $-1/Re$ | $1/Rm$ | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | $-1/R4$ | $1/R4$ | $1/Rb$ | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | $-1/Rb$ | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | -0.02 | -0.99 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | $1/Rc$ | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | $-1/Rc$ | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | -1 | 0.99 | 0 |
| 0 | 0 | 0 | 0 | $-1/Re$ | 0 | 0 | 0 | 0 | 0 | 0 | $1/Re$ | 0 | 0 | 0 | 0 | 0.02 | -1 | 0 |
| 0 | 0 | 0 | 0 | $-1/Rm$ | 0 | 0 | 0 | 0 | 0 | 0 | 0 | $1/Rm$ | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | -1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | -1 | -1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | -1 | 0 | 0 | 0 | 0 | 0 | 0 |

The G-Matrix is formed by considering all the resistors. In a closed network with various linear and nonlinear elements the G matrix represents the presence of resistors between various node.

C- Matrix

| | | | | | | | | | | | | | | | | | | |
|---|------------|------------------|---|-----------|---|--------------|---|---|---------------|------------|---|-----------|---|---|-----------|---|---|-----------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | C1 | -C1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | -C1 | Ccx+C1+C2 | 0 | 0 | 0 | 0 | 0 | 0 | -Ccx | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | C0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | | 0 | 0 | 0 | Cc+Ce | 0 | 0 | -Cc | -Ce | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | -Ccx | 0 | 0 | 0 | -Cc | 0 | 0 | Ccx+Ce | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | -Ce | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | Ce | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | Cm | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | Lc | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | Lm |

The C-Matrix is formed by considering all the capacitors and the inductors. In a closed network with various linear and nonlinear elements the C-matrix represents the presence of capacitors and the inductors between various node.

Source Vector $b(t)$

Diagram illustrating a bus structure $b(t)$ with 20 rows. The bus is represented by a vertical column of cells, alternating between shaded and unshaded rows. The values are:

- Row 1: 0
- Row 2: 0
- Row 3: 0
- Row 4: 0
- Row 5: 0
- Row 6: 0
- Row 7: 0
- Row 8: 0
- Row 9: 0
- Row 10: 0
- Row 11: 0
- Row 12: 0
- Row 13: 0
- Row 14: 0
- Row 15: Vdd
- Row 16: Vin
- Row 17: 0
- Row 18: Vdc
- Row 19: Vde
- Row 20: 0

The source vector represents the various voltage sources present in a network. It also denotes the node at which the source is present.

Function Vector $f(x(t))$

$f(x(t)) =$

$$\begin{pmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ g(V8-V7) + g(V9-V7) \\ -g(V8-V7) \\ g(V9-V7) \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

Nodes and their indices

| Node Label | Index Assigned by Hi-Spice |
|------------------|----------------------------|
| n _{dd} | 1 |
| n _{Vin} | 2 |
| n ₁ | 3 |
| n _{Vo} | 4 |
| A ₁ | 5 |
| n ₃ | 6 |
| xQ.n01 | 7 |
| xQ.n02 | 8 |
| xQ.n03 | 9 |
| xP.n04 | 10 |
| xQ.n05 | 11 |
| xCrystal.nC | 12 |
| xCrystal.C1 | 13 |
| V _{dd} | 14 |
| V _{in} | 15 |
| L _e | 16 |
| V _{dc} | 17 |
| V _{de} | 18 |
| L _m | 19 |

Table 1: Nodes in the network and their corresponding indices